
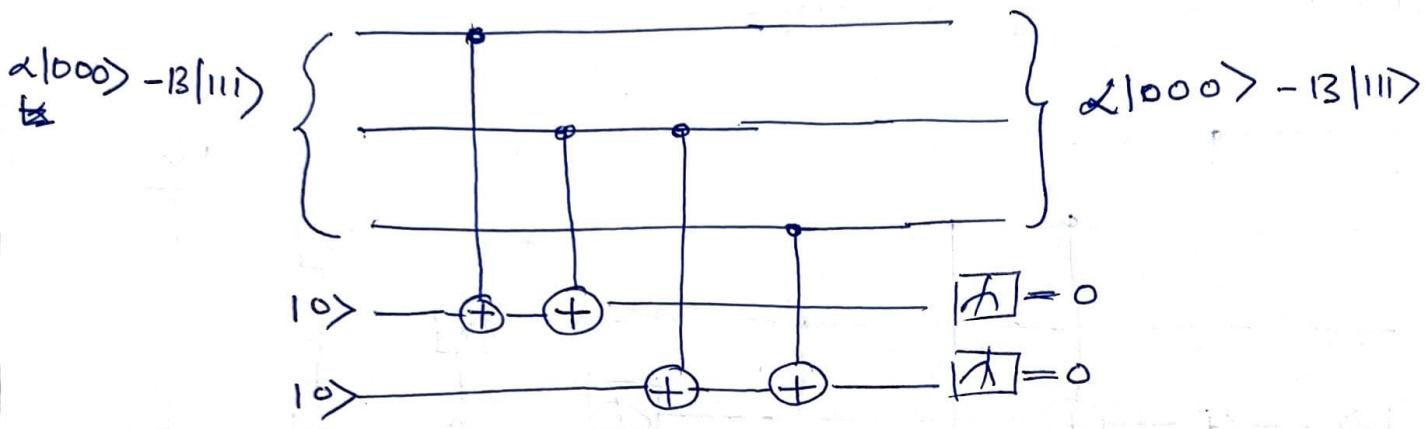


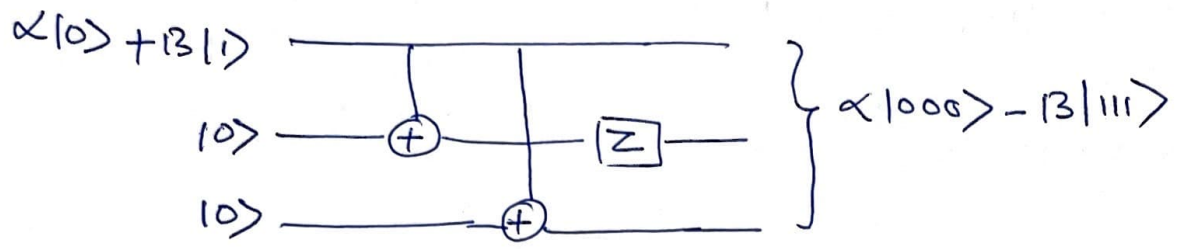
# Phase flip errors

- ✓ Bit-flip errors are not the only errors we need to worry about. But we also have phase flip errors described by Z-gate.
- ✓ Unfortunately the 3-bit repetition code fails to detect phase-flip errors. (As shown below)




- ✓ which wrongly suggests no errors
- ✓ So three bit repetition code helps to detect one bit bit-flip error but fails to detect phase-flip errors.

## Correcting phase-flip errors:

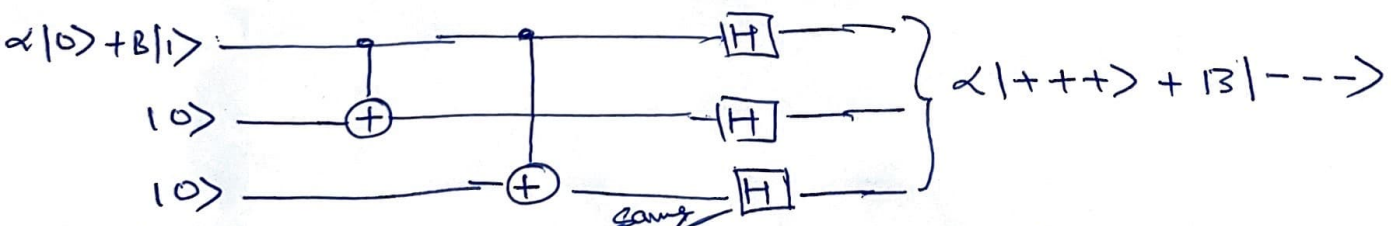


Hadamard gate converts 0 into +, + into -

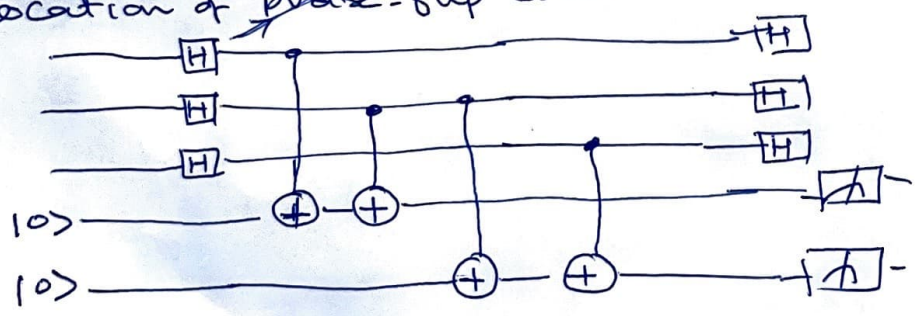Modifying the error detection circuit allows for the location of phase-flip error




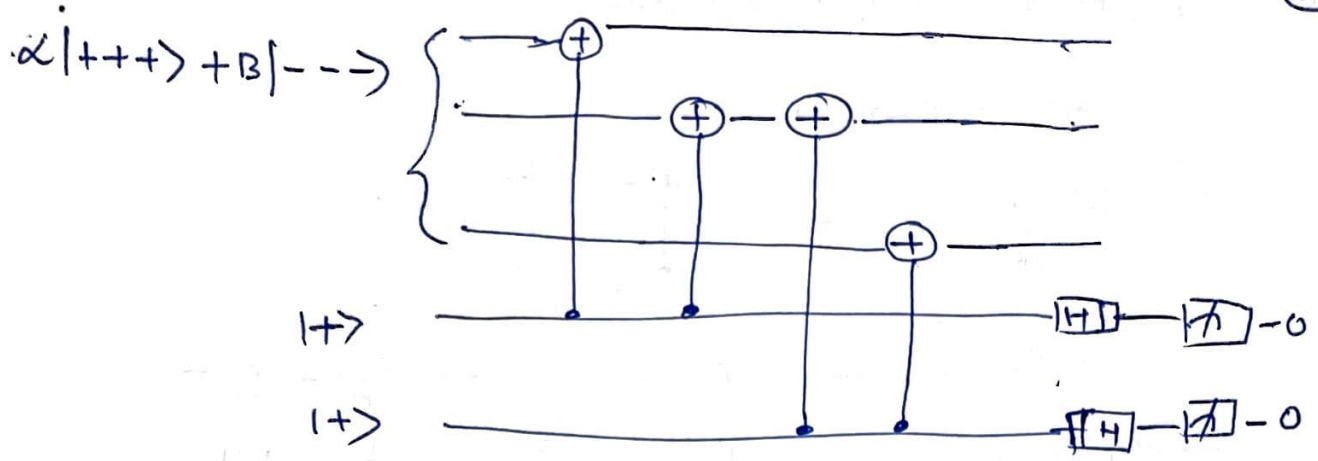Its Variant circuit is shown in next page



✓ If right most qubit phase flipped then output would be  $\alpha|++-> + \beta|--+>$  and the measurement be 1

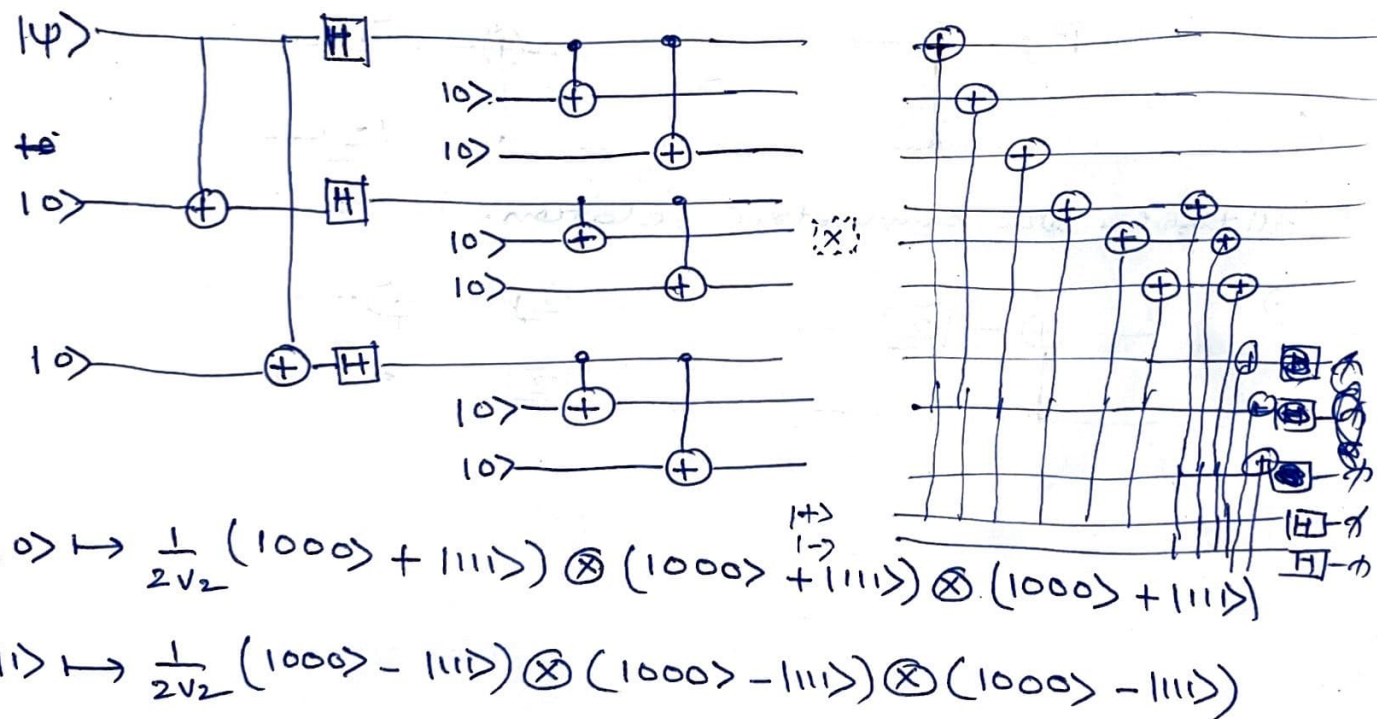Combining both bit-flip & phase-flip  $\Rightarrow$  9-qubit Shor Code  
9-qubit Shor Code:




- Bit-flip errors can be detected and corrected independently on each block by means of the inner code.
- We can correct even multiple bit-flips, provided there is only one bit flip in each block
  - Bit-flips and phase-flip can occur at same qubit, corrected completely independently




# Errors and C-NOTs relation.

## X and C-NOT relation

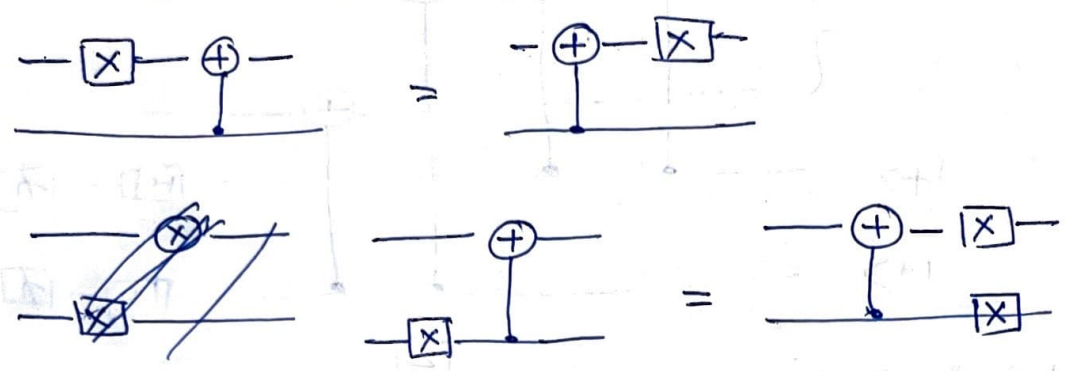

## Z and C-NOT relation

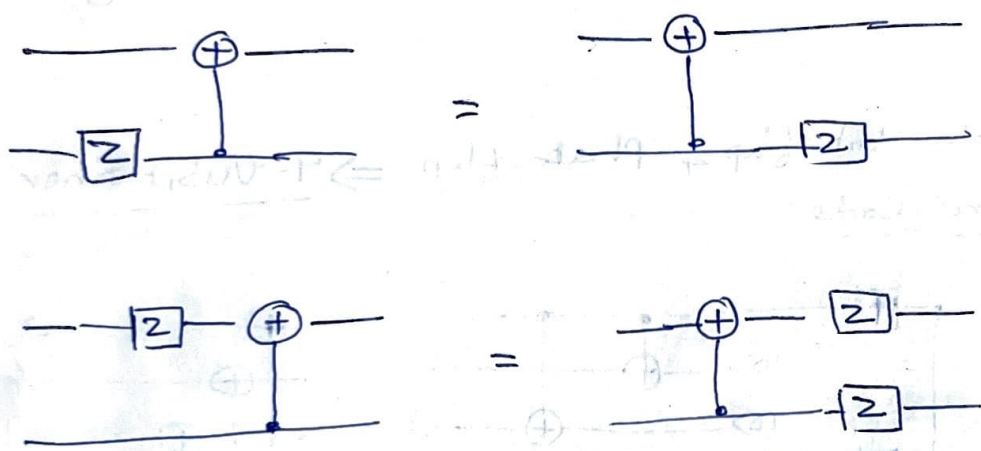

All these are symmetric relation. here

